

Demonstration of 10kW SiC Half Bridge DC/DC Converter

In PEE's Special Session at PCIM 2011 the results of a 10kW transformer isolated DC/DC converter using 1.7kV SiC MOSFETs were presented. The converter is a half-bridge topology operating at 32kHz hard-switched with a link voltage of 1kV. An efficiency of 97.1% was demonstrated and was achieved without extensive optimization. The characteristics of the 1.7kV SiC MOSFET, design details of the converter, and measured results are presented in this article. **Robert Callanan, Cree Inc., Durham NC USA**

The recent commercial introduction of the SiC MOSFET [1] represents one of the most significant advances in power electronics in the past 25 years. Simple topologies that have been considered impractical with Silicon switching components become practical with the SiC MOSFET.

This is especially true with the 1.7kV SiC MOSFET which has an unprecedented combination of low conduction loss and low switching loss. A key factor in accelerating the adoption of these devices is the ability to provide a generic but meaningful means of adequately demonstrating the key advantages of this technology. This means operating the device under full power conditions which



Figure 1: 1.7kV SiC MOSFET with 1.7kV, 10A JBS diode in TO-258 package co-pack

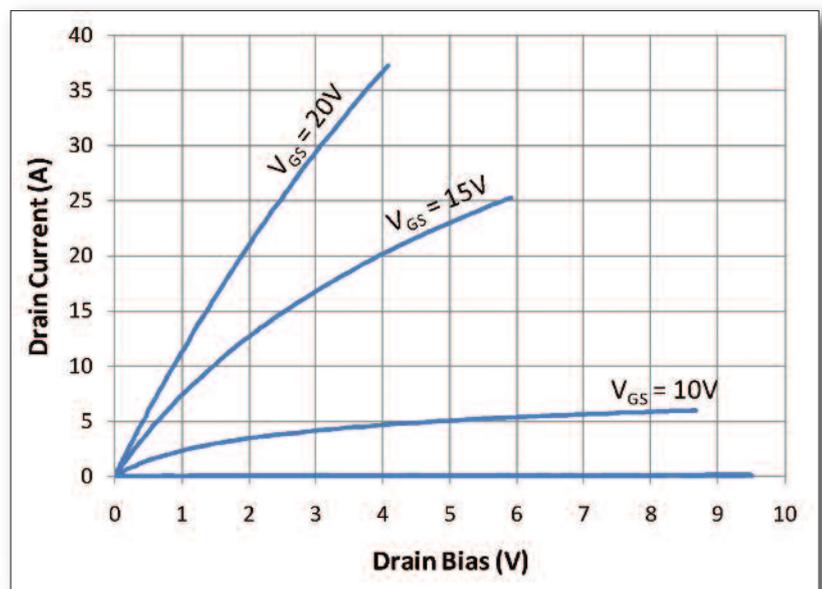


Figure 2: Forward I-V characteristics of 1.7kV MOSFET with V_{GS} of 0V, 5V, 10V, 15V and 20V

usually require the use of a high power source and load. Unfortunately, this is most inconvenient when the power levels are 10kW and above.

The approach taken in this work [2] was to construct a DC/DC converter and feed the output current back to the input similar to what is done for motor/drive testing. The converter delivers full power, but the power source need only deliver the circuit losses. This approach also gives a direct measurement of the total system power loss. Power conversion systems requiring 1.7kV switches typically utilize Si IGBTs or a multiplicity of Si MOSFETs. The switching loss of 1.7 kV Si IGBTs operating under hard switched conditions can efficiently operate at relatively low frequencies (~ 4kHz). Higher frequencies can be achieved by employing resonant topologies to mitigate the tail current losses. However, this requires additional resonant components and increases the RMS currents in the power components. Another alternative for 1.7kV high

frequency applications is to use multiple lower voltage Si MOSFETs in a multi-level topology. Hard switching was employed at 32kHz with a 1kV link to show high frequency operation under these conditions is easily achieved without reverting to resonant or multi-level techniques to achieve good efficiency at this operating frequency.

1.7kV SiC MOSFET

MOSFETs fabricated in 4H-SiC with capabilities for blocking in excess of 1.7kV and conducting 20A continuous current have been recently presented in the literature [3]. The switch consisted of a 1.7kV MOSFET and a 1.7kV 10A SiC JBS diode co-packed in a TO-258 package (see Figure 1). The DMOSFET die size is 4.08mm x 4.08mm, the JBS diode die size is 2.70mm x 3.81mm. The forward characteristics of the MOSFET are presented in Figure 2. The on-resistance of the device is less than 80 m Ω with 20V gate drive. Breakdown starts to occur at

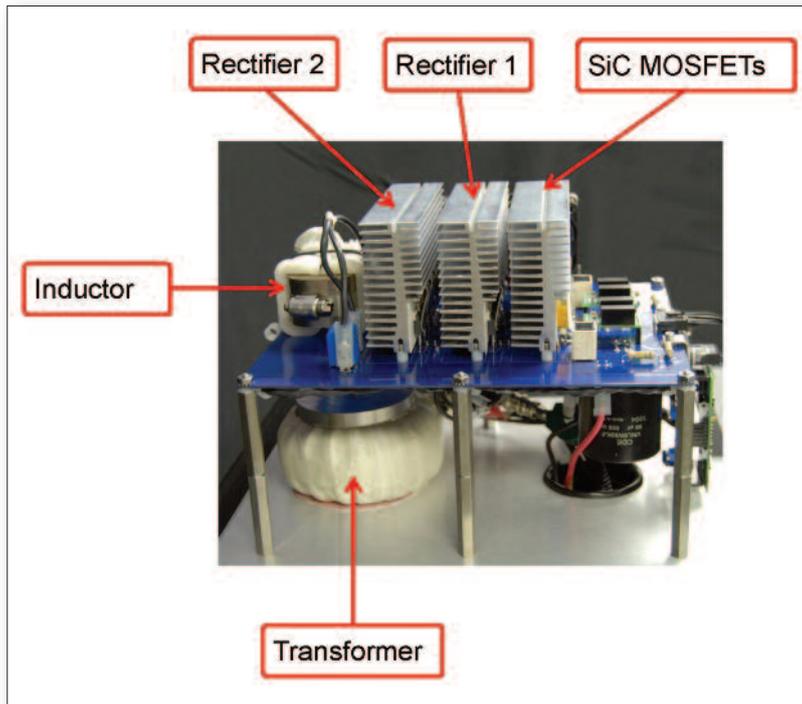


Figure 6: 10kW MOSFET demonstrator hardware

a nominal 10A DC. This results in 10kW of delivered power from only two SiC MOSFETs.

The actual hardware is shown in Figure 6. The power semiconductors are mounted on standard heat sink extrusions using forced air cooling. The 10kW step-up transformer employed a Vacuumschmelze T60004-L2080-W436 nanocrystalline toroid core. The dimensions of the core were ID=80mm, OD=63mm H=25mm with a cross sectional area of 1.62cm². The maximum operating flux density was 0.49T. The windings were comprised of Litz wire consisting of 210 strands of AWG 36 wire. The primary was 42 turns wound two in hand and the secondaries were 50 turns. Transformer cooling was accomplished by conduction to base plate. The output inductor L1 is 880µH and utilized a Metglas AMCC-32C core with 38 turns of the aforementioned Litz wire. No attempt made to mitigate effects of fringing flux. Cooling of the output inductor employed a combination of natural convection and a small amount of forced air.

Demonstrator results

The DC/DC converter delivered 10.44kW at 1kV DC with only 308W of loss. Figure 7 shows the output waveforms of the half-bridge inverter taken at the common point of MN1 and MN2. The blue waveform is the output voltage showing a 1.022kV

peak to peak amplitude. The red waveform is the output current showing 23.77 A RMS. The distribution of loss is listed in Table 1. The table lists measured loss as is and optimized loss with a few basic modifications.

The switching loss for both SiC MOSFETs was 34W and conduction loss was 42W for both devices. This equates to 17W switching loss and 21W conduction loss per SiC MOSFET (38 W total losses for each device). Note, the modest amount of SiC MOSFET switching loss shows that hard-switching operation at frequencies higher than 32kHz are definitely possible. The 60W of transformer loss breakdown was 10W core loss and 50W conductor loss.

The Litz wire was not selected for minimum loss. Therefore, a simple change in Litz wire design would result in a reduction of loss by perhaps 10W. The 112W of rectifier and snubber loss breakdown was 33W for each bridge and 46W for the snubber. This can obviously be improved by going to a single bridge with a more efficient snubber. The projected reduction in loss would be approximately 66W. The 56W of inductor loss breakdown was 39W core loss and 17W conductor loss. The 17W conductor loss breaks down to 5W for the DC current component and 12W for the AC component. As previously mentioned, no attempt was made to mitigate fringing flux effects. The inductor loss can be reduced by replacing the Metglas core with a nanocrystalline cut core and by using a multi-gapped design to minimize the fringing flux effects. These changes would reduce the inductor power loss by approximately 20W. The net effect of these modifications would reduce the total power loss from 308W to 212W with a resulting improvement of efficiency at 10.44kW from 97.1% to 98%. More aggressive techniques can be used to increase the efficiency further.

The SiC MOSFET heatsink temperature rise was only 28.8°C. The worst case rectifier heat sink rise was only 17.1°C. The hottest component was the transformer. An experiment was done where forced convection cooling was used and the transformer surface temperature dropped to approximately 38°C, only 13°C temperature rise.

Conclusions

The 1.7kV SiC MOSFET has an unprecedented combination of low conduction loss and switching loss. The demonstrator shows how two of these

Figure 7: Half-bridge inverter output waveforms at 32kHz (blue = voltage 500V/div, red = current 20A/div, time = 20µs/div)

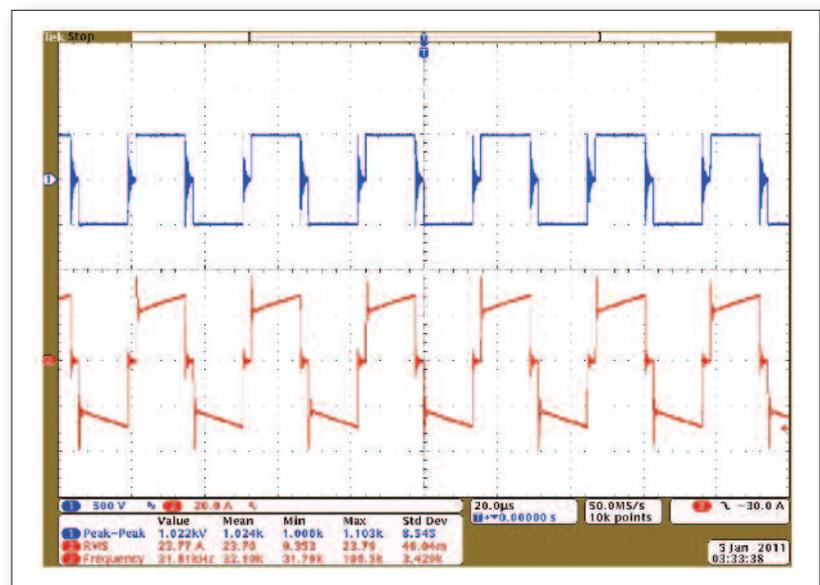


Table 1: Loss distribution of 10kW SiC DC/DC converter

Component	Loss	
	Measured	Optimized
SiC MOSFETs Switching	38 W	38 W
SiC MOSFET Conduction	42 W	42 W
Transformer	60 W	50 W
Rectifiers & Snubbers	112 W	46 W
Inductor	56 W	36 W
Total Loss	308 W	212 W
Efficiency @ 10.44kW	97.1%	98%

1.7kV SiC MOSFETs can easily realize a 10kW, 1kV hard-switched DC/DC converter operating at 32kHz with an efficiency of 97.1% without extensive optimization. Higher efficiency can be achieved through some basic modifications. The modest switching loss of the SiC MOSFET allows higher switching frequencies using hard-switched topologies is definitely possible. This technology enables substantial improvements in size, weight, and efficiency in all aspects of power conversion such as 690V motor drives,

auxiliary power converters for traction, solar inverters and wind applications to name a few. This performance utilizing a very simple and robust half-bridge hard-switched topology would be difficult, if not impossible, using Silicon IGBTs.

Literature


[1] "First Commercial Silicon Carbide Power MOSFET Launched by Cree", *Power Electronics Europe 1/2011*, pages 21-22.

[2] R. Callanan, "Demonstration of


1.7kV SiC DMOSFETs in a 10kW, 1kV, 32kHz Hard-Switched Half Bridge DC-DC Converter", *PEE Special Session "High Frequency Switching Devices and Applications" at PCIM 2011, Nuremberg, Germany*

[3] B. A. Hull, S.-H. Ryu, J. Zhang, C. Jonas, M. O'Loughlin, R. Callanan, and J. Palmour, "1700V, 20A 4H-SiC DMOSFETs Optimized for High Temperature Operation", *8th European Conference on Silicon Carbide and Related Materials 2010, Oslo, Norway*.

Looking for
High Performance ULDOs?

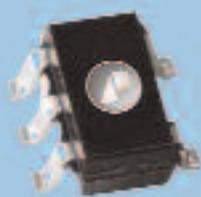

SOT-23-5

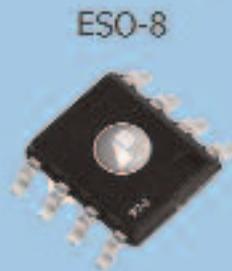

ESO-8

**More Ultra Low Drop-out
Linear Regulators Now Available**

RoHS/REACH-compliant, halogen-free
Broad range of industry-standard package types
Drop-out voltage at full load as low as 120mV

APUB851Y5-HF-3	120mV drop-out at 100mA, SOT-23-5
APU1205Y5-HF-3	270mV drop-out at 300mA, SOT-23-5
APE1180-HF-3	200mV at 1.5A, TO-252/220/263-5
APE8903BMP-HF-3	230mV drop-out at 2A, ESO-8
APE8906MP-HF-3	280mV drop-out at 3A, ESO-8
APU11755-HF-3	500mV drop-out at 7.5A, TO-263-5

More parts at www.a-powerusa.com/uldo

Advanced Power Electronics Corp. USA
3150 Almaden Expressway • San Jose CA 95118
+1(408) 717-4231 • Sales@a-powerusa.com

To receive your
own copy of

**POWER
ELECTRONICS**

EUROPE

subscribe today at:

www.power-mag.com